

Analysis of electric power and energy systems

Lecture 4: Transformers, power flow analysis part 2

Bertrand Cornélusse
bertrand.cornelusse@uliege.be


What will we learn today?

- The power transformer
- The next part of power flow analysis: how to include transformers, and transformers with tap changers

You will be able to do exercises 6.2, 6.3, 6.4 from the Ned Mohan's book.

The transformer

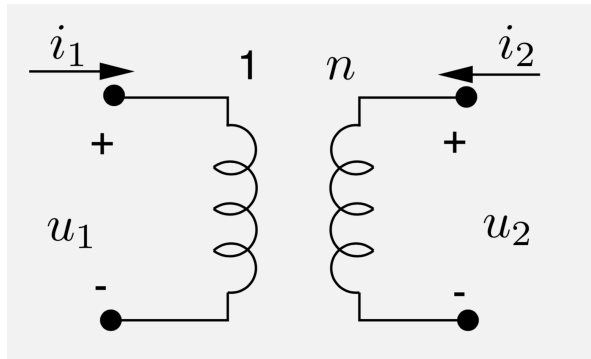A (single phase) transformer is made of two magnetically coupled coils or windings. An ideal transformer is a two-port represented as



with

$$u_2 = nu_1$$

$$i_2 = -\frac{1}{n}i_1$$

In power systems, transformers are mainly used to transmit power over long distances by changing the voltage level, thus decreasing the current for a given power level. Voltage level of synchronous generator around 20kV.

Voltage is changed around 5 times between generation and load.

It is also used to **measure** currents and voltages, electrically **isolate** parts of a circuit (not the auto-transformer we will see), **match** impedances.




How does a Transformer work ?




Watch later



Share

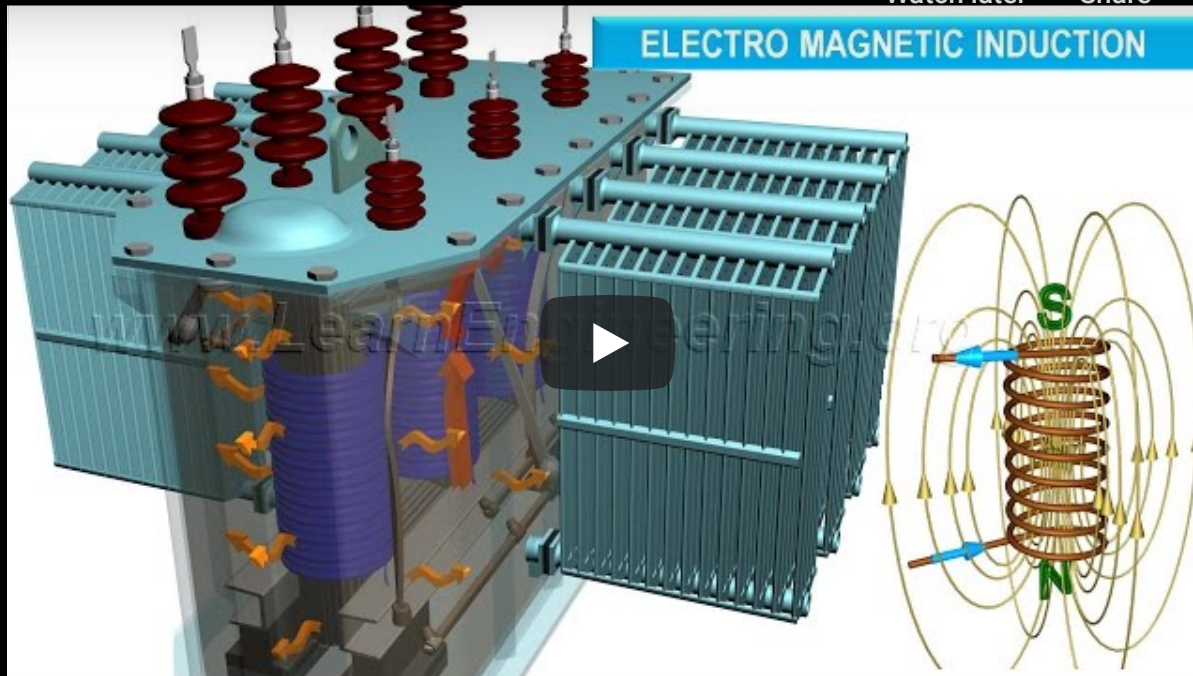

Non-ideal model

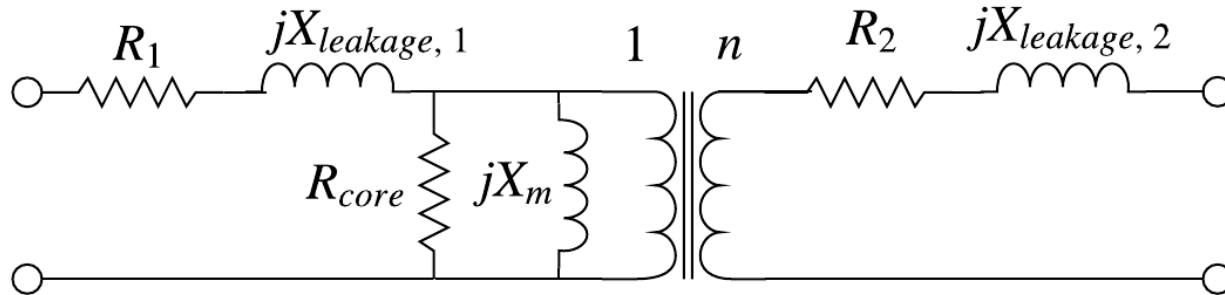


The ideal model is complemented by elements

- X_m that models the magnetizing inductance
- $X_{leakage, i}$ that models the flux not captured by the core on side i
- R_{core} that models eddy current and hysteresis losses, i.e. losses in the iron core
- R_1 and R_2 that model (coil) copper losses

Parameters are either given in the datasheet or obtained by open-circuit and short-circuit tests.

Laminated core to decrease losses.

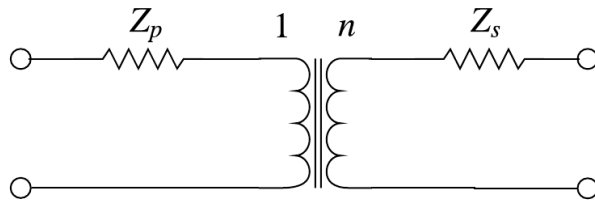The excitation current, sum of the currents in R_{core} and X_m , is often neglected, leading to a simpler non-ideal model, and the series impedances can be transferred from one side to the other:





with

$$Z_p = R_1 + jX_{leakage,1}$$

and

$$Z_s = R_2 + jX_{leakage,2}$$

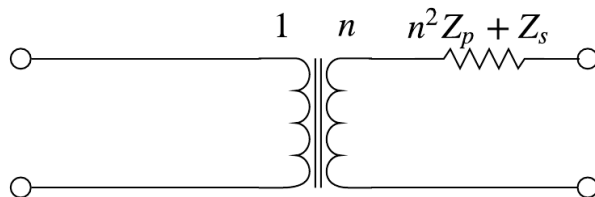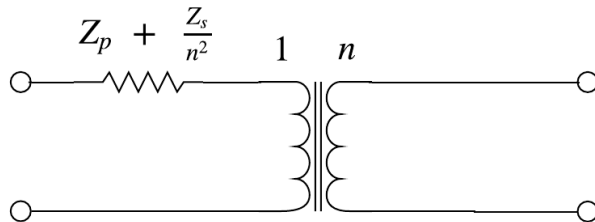

Per unit representation

Let's consider the rated voltages and currents on both sides of the (ideal) transformer as base values. As

$$V_{s,base} = nV_{p,base}$$

and


$$I_{p,base} = nI_{s,base},$$

the MVA base is the same on both sides, and thus

$$Z_{s,base} = n^2 Z_{p,base}$$

Hence, in per unit, the transformer can be replaced by a single impedance
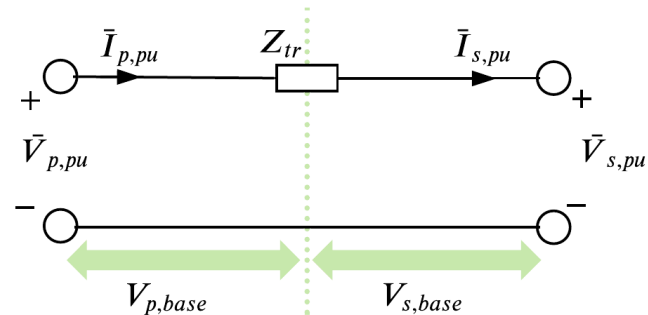
$$Z_{tr} = \frac{Z_p}{Z_{p,base}} + \frac{Z_s}{Z_{s,base}}.$$



Thus we have also that


$$\begin{aligned} Z_{tr} &= \frac{Z_p + Z_s/n^2}{Z_{p,base}} \\ &= \frac{n^2 Z_p + Z_s}{Z_{s,base}} \end{aligned}$$

i.e. the impedance is the same whether we see it from the primary or the secondary side, although the voltage bases differ.

Also, if the three-phase transformer is wye-delta connected, a 30° phase shift must be applied (more on this later).

Example 6.1

Consider the one-line diagram

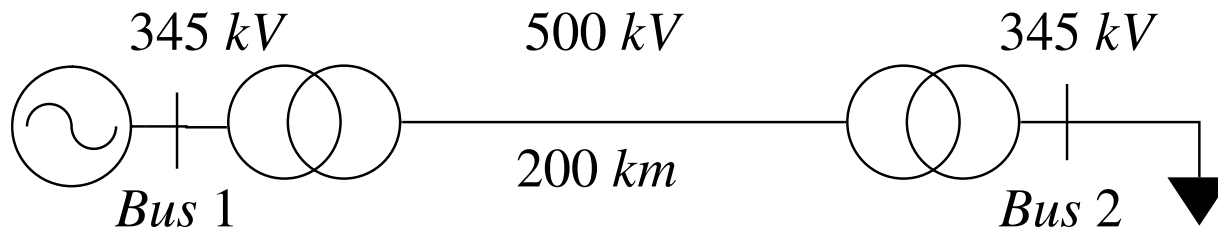

with

- a 200 km line with $R = 0.029\Omega/km$, $X = 0.326\Omega/km$, neglected shunt impedances
- two transformers with a leakage reactance of $0.2pu$ in the (500 kV, 1000 MVA) base, and losses neglected.

What is the equivalent model in a (345 kV, 100 MVA) base?

In the (500 kV, 1000 MVA) base:

-

$$Z_{line,pu} = 200 \times (0.029 + j0.326)/(500^2/1000) = 0.0232 + j0.2608pu$$

- hence the total impedance between buses 1 and 2 is

$$Z_{12} = 0.0232 + j0.2608 + 2 * j0.2pu = 0.0232 + j0.6608pu$$

In the (345 kV, 100 MVA) base:

- the pu value of the impedance is the same in the (500 kV, 1000 MVA) and (345 kV, 1000 MVA) bases,
 - since we can transfer the impedance from one side of each transformer to the other, cf. a previous remark
- if we now change the MVA base to 100 MVA,

$$Z_{12} = 0.0232 + j0.6608 \times (100/1000)pu = 0.00232 + j0.06608pu$$

since the base impedance is proportional to the inverse of the MVA base.

Efficiency

The efficiency expressed in % is

$$100 \times \frac{P_{output}}{P_{input}} = 100 \times \left(1 - \frac{P_{losses}}{P_{input}} \right)$$

- maximal when copper losses = iron losses (cancel derivative of efficiency w.r.t current)
- Around 99.5 % in large power transformers at full load.

Tap changers

- Some transformers are equipped with a system allowing to change the $1 : n$ ratio
- The ability to change the tap under load is called load tap changer (LTC) or on-load tap changer (OLTC)
- This is mainly used for voltage control
- It is usually implemented using auto-transformers
- We will see later on how to include this in the power flow analysis




On Load Tap Changer :- How it works?



Watch later



Share

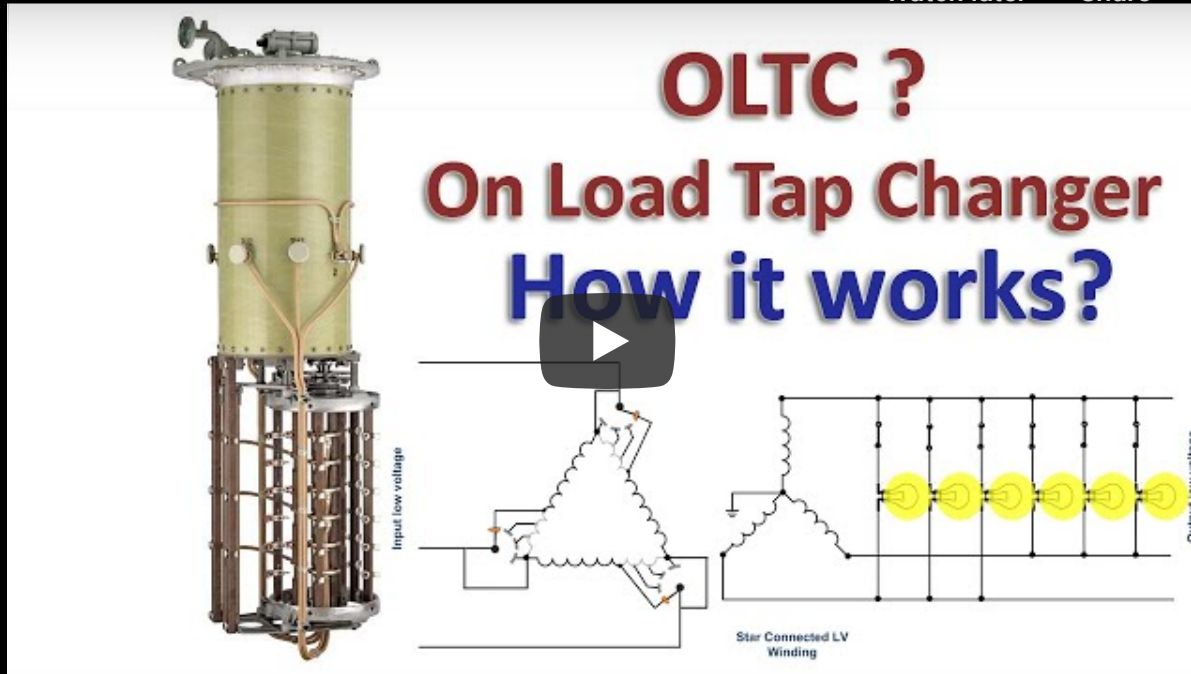

Auto-transformers

The two windings (of the same phase) are connected in series, without galvanic insulation. They are commonly used when the ratio is limited.

Advantages:

- Physically smaller
- less costly (less copper)
- higher efficiency
- easy to implement tap changes
- "solid" earth grounding

Disadvantages:

- no electrical insulation
- higher short circuit current
- full voltage at secondary if it breaks (in case of a step down)



Auto Transformer working principle, how Var...



Watch later




Share

Auto Transformer's Concept & Use



G K Agrawal

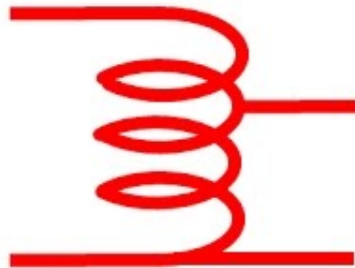


Phase shift in delta-star transformers

The star part has n times the number of turns of the delta part (primary side).

Let's reason on phase a ,

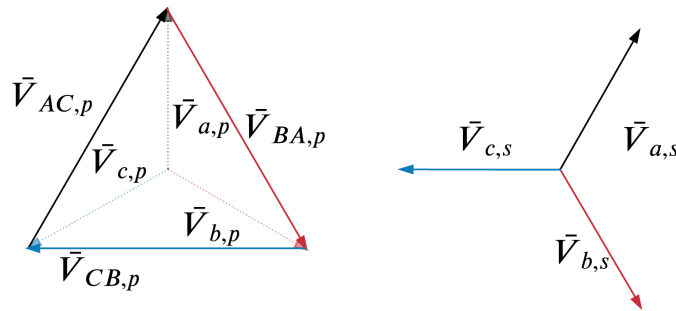- Voltage $\bar{V}_{a,s}$ is on the same core as $\bar{V}_{AC,p} = \sqrt{3}\bar{V}_{a,p} \angle -30^\circ$ where $\bar{V}_{a,p}$ is the (virtual) phase-neutral voltage on the primary side.
- Since $\bar{V}_{a,s} = n\bar{V}_{AC,p}$, $\bar{V}_{a,s} = n\sqrt{3}\bar{V}_{a,p} \angle -30^\circ$




We gain a $\sqrt{3}$ factor in the amplification, but a lagging phase shift of 30° .

The same reasoning holds for phases b and c .

Power flow regulation by phase shifting

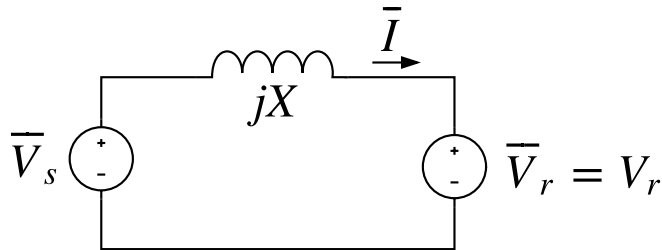We have seen in [lecture 2](#) that active power flows are dictated by the voltage magnitudes but also the sine of the angle difference between buses:



$$\begin{aligned} S_r &= \bar{V}_r \bar{I}^* = V_r \left(\frac{V_s \angle -\delta - V_r}{-jX} \right) \\ &= \frac{V_s V_r \sin \delta}{X} + j \frac{V_s V_r \cos \delta - V_r^2}{X} \end{aligned}$$

δ is the angle between \bar{V}_r and \bar{V}_s

If we have a device that can generate an adjustable phase shift, we can control the power flows. This is the purpose of [phase-shifting transformers](#).

In practice phase shifting is achieved by "combining the signal with a fraction of itself shifted by 90°". For the details of how it is implemented or modeled, see


- [Wikipedia](#)
- Section 5.7. of the Weedy or ELEC0014.
- [ENTSO-E - Phase Shift Transformers Modelling, Version 1.0.0, May 2015](#)

Example: phase shifting transformers on the borders of Belgium



380/380 kV : in series with:

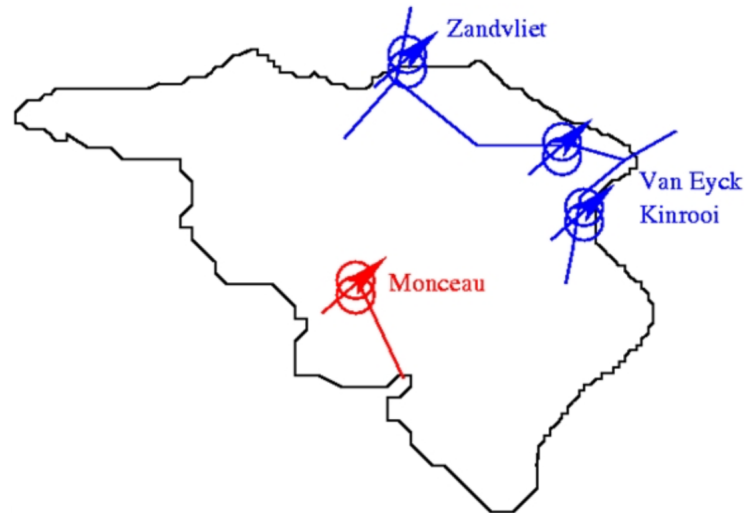1. line Zandvliet (B) - Borssele (NL) and Zandvliet (B) - Geertruidenberg (NL)
2. line Meerhout (B) - Maasbracht (NL)
3. line Gramme (B) - Maasbracht (NL)
 - nominal power $3V_N I_{max} = 1400 \text{ MVA}$
 - phase shift adjustment: 35 positions, $+17/-17 \times 1.5^\circ$ (at no load)



220/150 kV :

- in series with the Chooz (F) - Monceau (B) line nominal power: 400 MVA
- in-phase adjustment : 21 positions, $+10/-10 \times 1.5 \%$
- quadrature adjustment: 21 positions, $+10/-10 \times 1.2^\circ$

Remarks

In **three-phase operation**,

- either there are three separate single-phase transformers (easier to fix when there is a problem on a phase, more modular)
- or a **three-phase transformer**, that is a single core with three auto-transformers on it, cf. the video at the beginning of this presentation (cheaper, lighter core and less copper).

Some transformers called **three-winding transformers** are equipped with a third winding (not to be confused with a three-phase transformer) that is used for auxiliary purposes (feeding auxiliary devices e.g. fans, providing reactive power support, ...)

Transformers in the power flow analysis

Transformer without regulation


A transformer, in the per unit representation, can thus be represented

- as a two-port if the shunt admittance are considered
- as a simple series leakage impedance if the shunt admittance is neglected

Representing taps and phase shifts

Let \bar{Y}_l be the leakage admittance and \bar{t} be the off-nominal turns ratio:

- if $0 < \bar{t} \leq 1$, this corresponds to a simple tap-changer
- if $0 < |\bar{t}| \leq 1$ but is complex, then this is a phase-shifter ($\angle \bar{t} < \pi/2$)

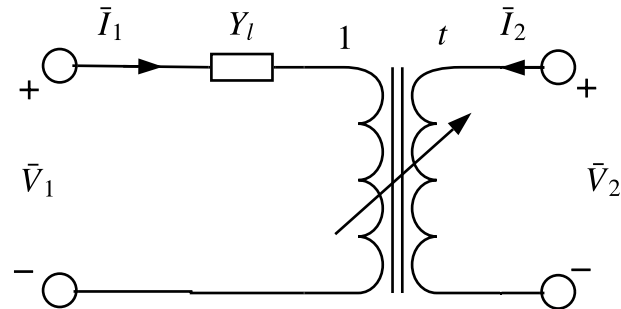

We have

$$\bar{I}_1 = \left(\bar{V}_1 - \frac{\bar{V}_2}{\bar{t}} \right) \bar{Y}_l$$

and since $\frac{\bar{V}_2}{\bar{t}} \bar{I}_1^* = \bar{V}_2 \bar{I}_2^*$ by energy conservation

$$\bar{I}_2 = -\frac{\bar{I}_1}{\bar{t}^*} = -\bar{V}_1 \frac{\bar{Y}_l}{\bar{t}^*} + \bar{V}_2 \frac{\bar{Y}_l}{|\bar{t}|^2}$$

Thus tap and phase shift can be represented by the admittance matrix

$$\begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \end{bmatrix} = \begin{bmatrix} Y_l & -\frac{Y_l}{t} \\ -\frac{Y_l}{t^*} & \frac{Y_l}{|t|^2} \end{bmatrix} \begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix}$$

- if $0 < t \leq 1$, this can be represented as a π two-port
- if $0 < |t| \leq 1$ but is complex, this is not the case

In the **power flow analysis**, you must **pay attention to this** when constructing the **system-wide admittance matrix**.

Pandapower example

See python notebook / video recording.

References

- Mohan, Ned. Electric power systems: a first course. John Wiley & Sons, 2012. Chapter 6.
- Weedy, Birron Mathew, et al. Electric power systems. John Wiley & Sons, 2012. Section 3.8, Section 5.7.
- [Course notes of ELEC0014](#) by Pr. Thierry Van Cutsem.

